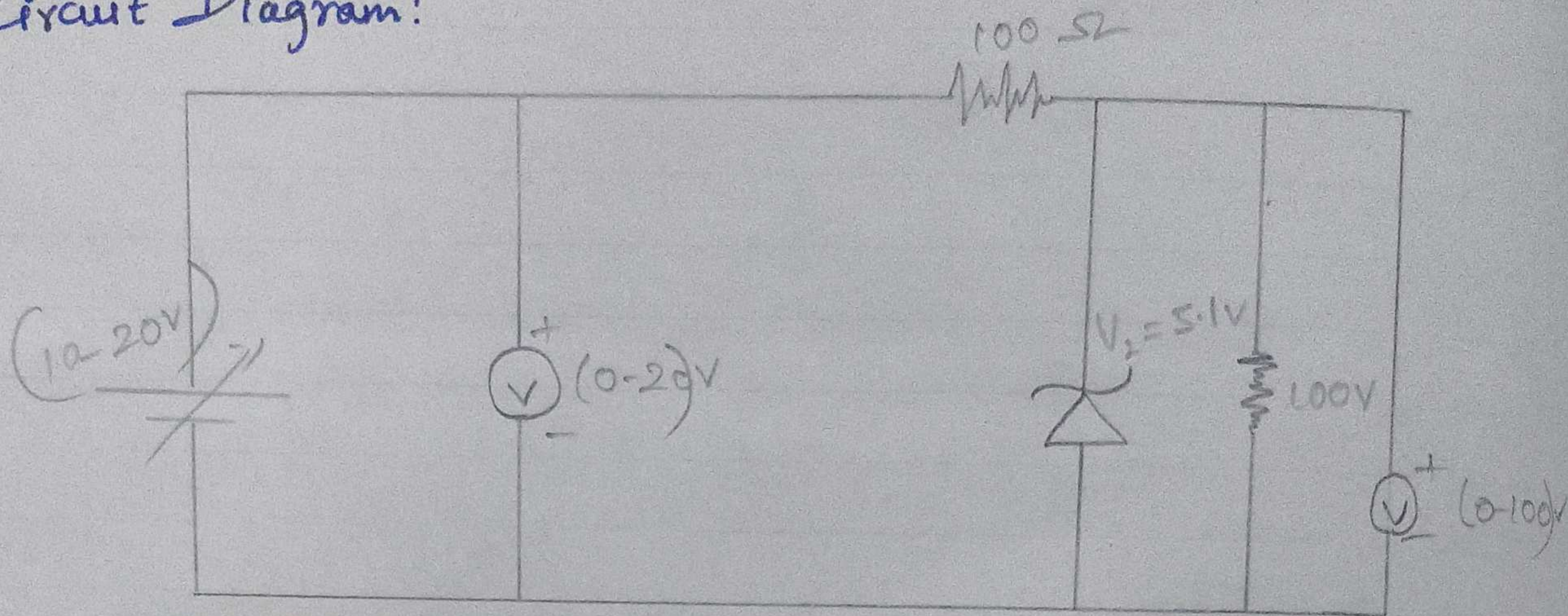


Line Regulation:

Circuit Diagram:



Tabulation:

Sl No.	Input voltage V_1 (V)	Output voltage (V)
1	+12.0	+5.14
2	+13.0	+5.16
3	+14.0	+5.17
4	+15.0	+5.17
5	+16.0	+5.18
6	+17.0	+5.19

Model Graph:

Output
Voltage
 V_o (V)

Load Resistance

09/3/26

Zener diode as voltage Regulator.

Aim:

To simulate the line and load regulation operation zener diode.

Apparatus Required:

Laptop with proteus Software.

Theory:


A heavily doped PN Junction diode is called zener diode. Due to heavily doped nature zener diode works under forward bias and reverse bias conditions.

Zener diode under reverse bias condition is used as a voltage regulator. Even if input voltage changes the output is constant. This is called line regulation.

If the load resistance changes the output voltage is constant. This is called load Regulation.

Load Regulation:


Circuit Diagram:

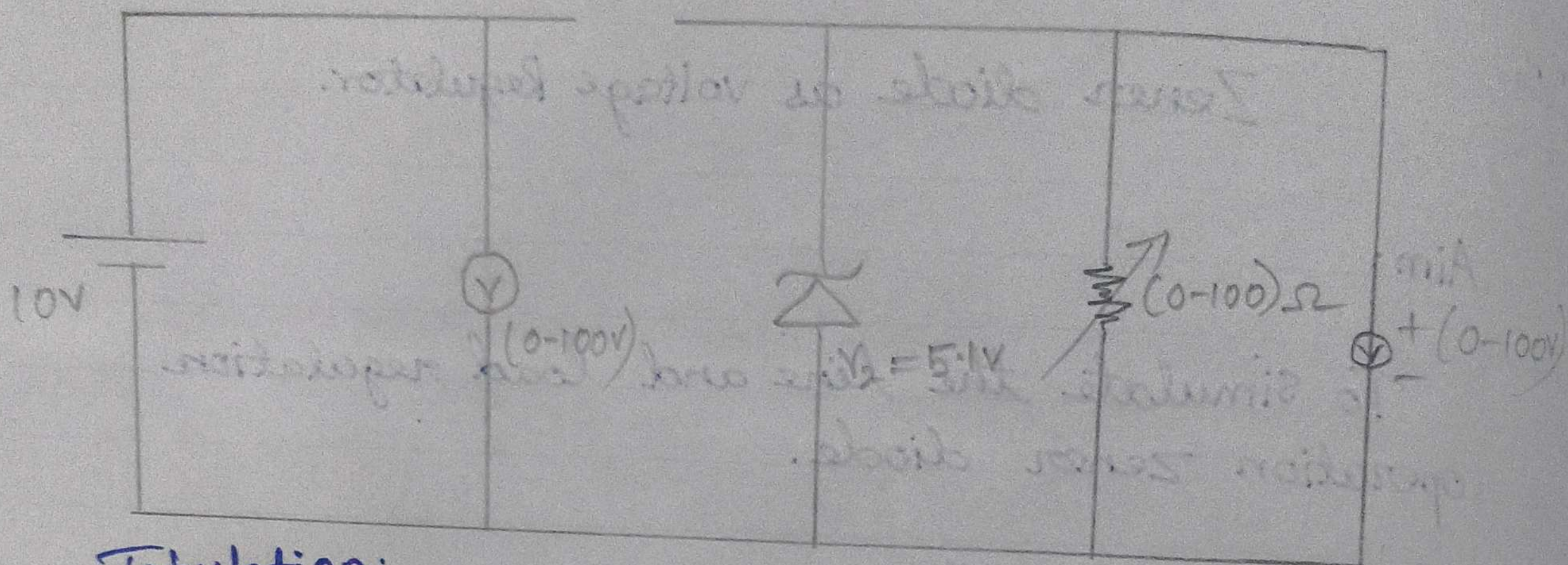

Tabulation:

Sl. No.	Load Resistance $R_L(\Omega)$	Output Voltage $V_o (v)$
1	100 Ω	+5.19
2	200 Ω	+5.20
3	300 Ω	+5.20
4	400 Ω	+5.20
5	500 Ω	+5.20
6	600 Ω	+5.21

Model Graph:

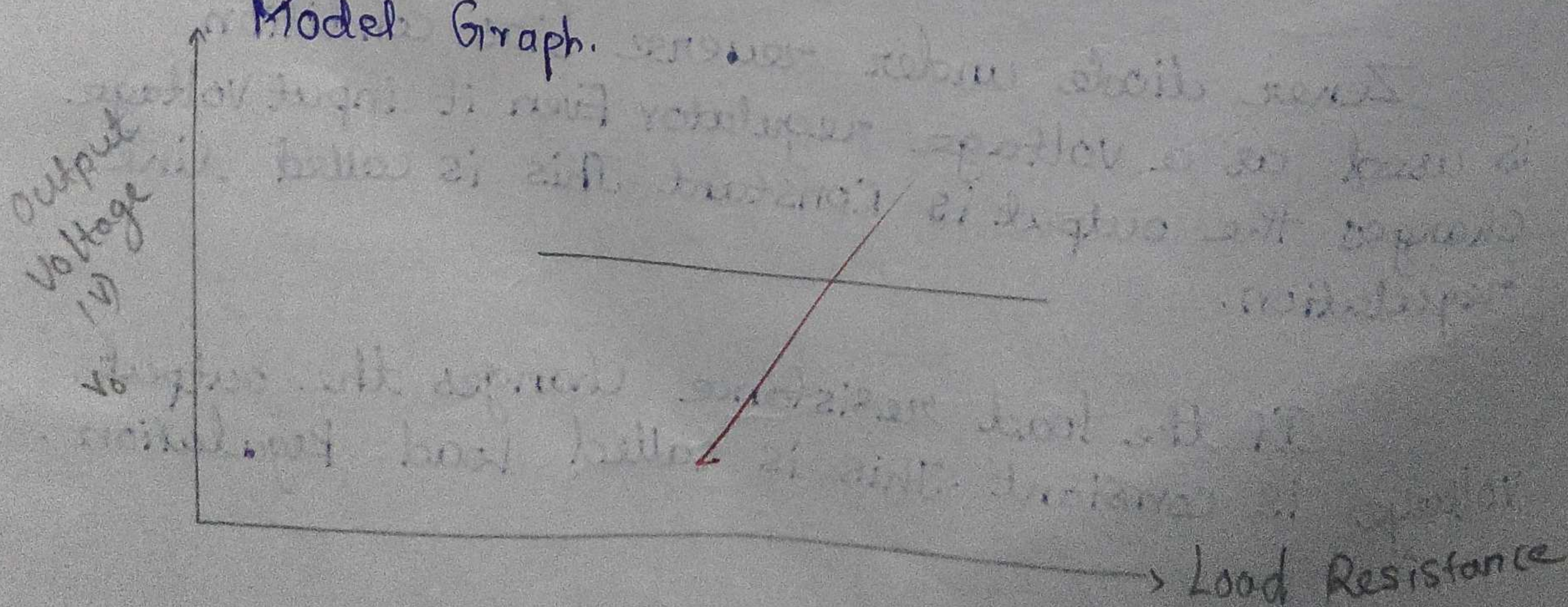

Procedure:


1. Drag the required components from the proteus library.

2. Connect the components (required) as per circuit diagram.

3. For line regulation vary the input voltage and note the output voltages in tabulation. Draw the graph between input and Output voltages.

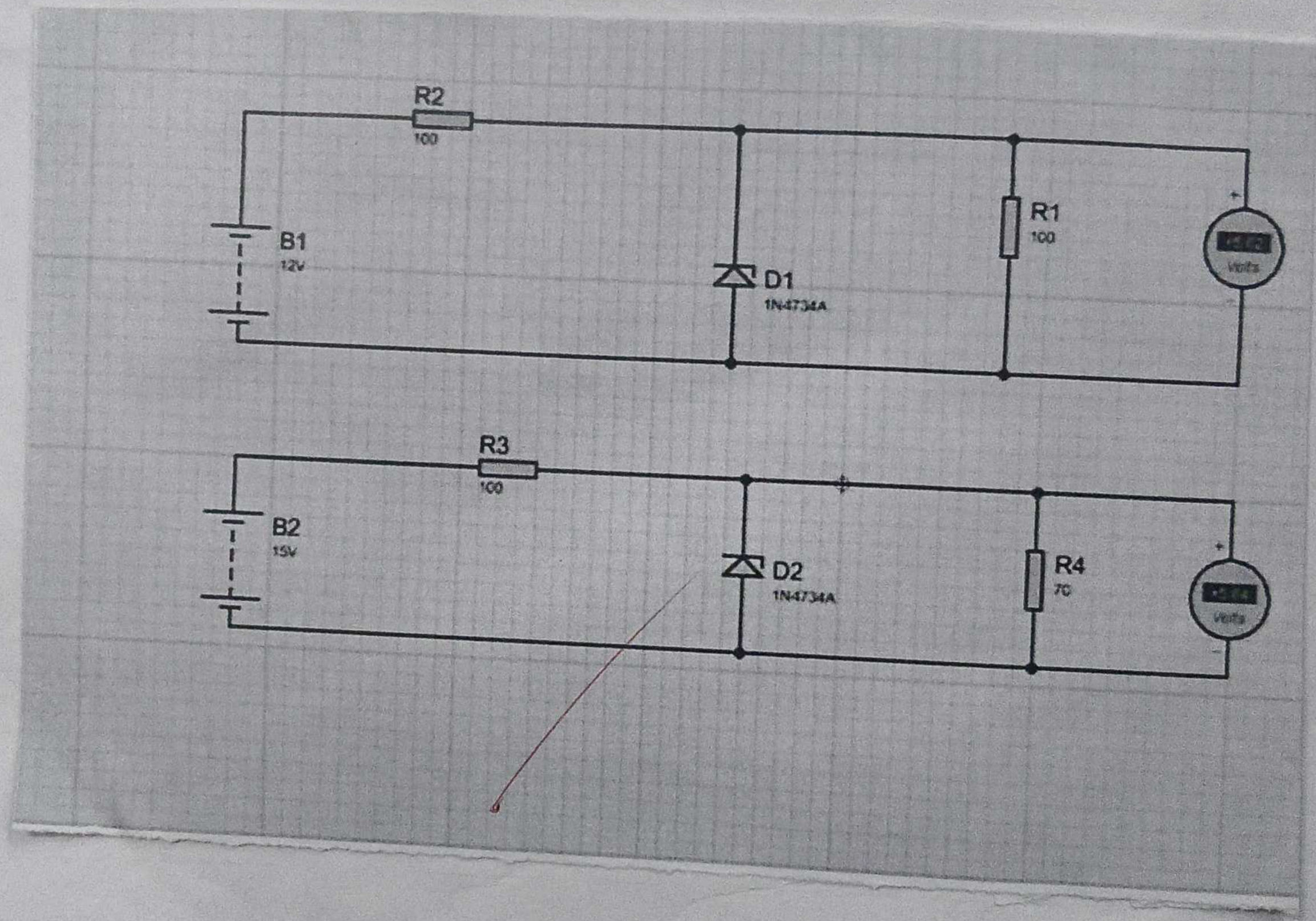4. For load regulations vary the load resistance and note the output voltage in tabulation. Draw the graph between load resistance and output voltage.

Handwritten notes on the notebook page above the circuit diagram, including the word "circuit" and some illegible text.





✓ 18/03/20

Result:

Thus stimulation of line load regulation.
operation of Zener diode Success fully completed.